Dane aktualne na dzień: 19-11-2026 23:54

Link do produktu: https://www.minicena.pl/sygnalizacja-swietlna-led-dla-dzieci-zestaw-mlody-elektryk-zabawka-do-nauka-p-682.html



SYGNALIZACJA ŚWIETLNA LED DLA DZIECI ZESTAW MŁODY ELEKTRYK ZABAWKA DO NAUKA

Cena	**21,47 zł**
Numer katalogowy	**Zestaw doświadczalny**
Kod producenta	**Zestaw doświadczalny**
Kod EAN	**5905858682406**
Wiek dziecka	**8 lat +**
Certyfikaty, opinie, atesty	**CE**
Kod producenta	**Zestaw doświadczalny**
Szerokość produktu	**22**
EAN (GTIN)	**5905858682406**
Baterie	**Baterie 3x AA**
Marka	**bez marki**
Materiał	**karton**
Minimalny wiek dziecka	**8**
Wysokość produktu	**12.5**
Głębokość produktu	**3.5**
Kolor	**wielokolorowy**
Rodzaj	**mały elektronik**

Opis produktu

SYGNALIZACJA ŚWIETLNA LED DLA DZIECI ZESTAW MŁODY ELEKTRYK ZABAWKA DO NAUKA

- Zestaw doświadczalny dla młodego elektryka / mechanika.

Edukacja przez zabawę jeszcze nigdy nie była tak interesująca!

Zestaw sygnalizacji świetlnej Młody Elektryk to idealna zabawka dla dzieci, które chcą poznawać podstawy ruchu drogowego w sposób interaktywny i w pełni bezpieczny.

Zabawka jest doskonałym narzędziem edukacyjnym – wprowadza dzieci w świat znaków drogowych, kolorów sygnalizacji świetlnej oraz zasad bezpieczeństwa, które będą im towarzyszyć przez całe życie.

Jak działa sygnalizacja świetlna??

- Zestaw do eksperymentów naukowych.

Zestaw z sygnalizacją świetlną umożliwia dzieciom wykonywanie według instrukcji podłączania obwodów / sprzączek, aby zasilić sygnalizację świetlną.

Zasilanie bateriami 3x AA (brak w zestawie)

Zestaw zawiera:

- wszystkie części i akcesoria niezbędne do przeprowadzenia doświadczeń, instrukcję obsługi

Naucz dziecko zasad ruchu drogowego z zestawem sygnalizacji świetlnej Młody Elektryk! Realistyczne efekty LED, rozwijają wyobraźnię i wiedzę o bezpieczeństwie. Idealny prezent edukacyjny!

Zestaw zapakowany w kolorowe opakowanie kartonowe, które świetnie nada się na prezent.

- **certyfikat:** CE
- **wiek:** 8 +
- **wymiar opakowania:** 22 x 12,5 x 3,5cm


SCIENCE
EXPERIMENT
TO IMAGINE
STEAM
PUZZLE GAMES
TRAFFIC LIGHTS
BUCKLE
CIRCUITS
8+
OFF
ON
15
14
As shown in the figure,Turn on the switch 15, the traffic light L1 will start. The time of red and green is 9 seconds respectively, and the time of yellow is 3 seconds.
Press the press switch 14 , will switch to the next light.
-01-


SCIENCE
EXPERIMENT
TO IMAGINE
STEAM
PUZZLE GAMES
TRAFFIC LIGHTS
BUCKLE
CIRCUITS
8+
OFF
ON
15
14
As shown in the figure,Turn on the switch 15, the traffic light L1 will start. The time of red and green is 9 seconds respectively, and the time of yellow is 3 seconds.
Press the press switch 14 , will switch to the next light.
-01-


SCIENCE
EXPERIMENT
STEAM
TRAFFIC LIGHTS
BUCKLE
CIRCUITS


icreate


SCIENCE
EXPERIMENT
STEAM
BUCKLE
CIRCUITS
8+
TRAFFIC LIGHTS
OFF
ON
15
14
4.5V
TRAFFIC LIGHTS


SCIENCE
EXPERIMENT
BUCKLE
CIRCUITS
TRAFFIC LIGHTS
DEVELOP THINKING
MAGINATION
IGNITE INSPIRATION!
STEAM
OFF
ON
4.5V
TRAFFIC LIGHTS
NO.450


2
4
4.5V
15
ON
OFF
14


SCIENCE
EXPERIMENT
TO IMAGINE
STEAM
PUZZLE GAMES
TO IMAGINE
BUCKLE
CIRCUITS
TRAFFIC LIGHTS
8+
AGES


SCIENCE
EXPERIMENT
TO IMAGINE
STEAM
PUZZLE GAMES
TO IMAGINE
TRAFFIC LIGHTS
BUCKLE
CIRCUITS
8+
AGES
EXPERIMENT
OFF
ON
15
14
As shown in the figure, Turn on the switch 15, the traffic light L1 will start. The time of red and green is 9 seconds respectively, and the time of yellow is 3 seconds.
Press the press switch 14, will switch to the next light.
-01-


SCIENCE
EXPERIMENT
SCIENCE
EXPERIMENT
TO IMAGINE
STEAM
PUZZLE GAMES
TO IMAGINE
TRAFFIC LIGHTS
BUCKLE
CIRCUITS
8+
TRAFFIC LIGHT
EXPERIMENT
As shown in the figure,Turn on the switch 15, the traffic light L1 will start. The time of red and green is 9 seconds respectively, and the time of yellow is 3 seconds.
Press the press switch 14, will switch to the next light.
-01-
OFF
ON
15
14
4.5V
2
4


SCIENCE
EXPERIMENT
TO IMAGINE
STEAM
PUZZLE GAMES
BUCKLE
CIRCUITS
TRAFFIC LIGHTS
8+
OFF
ON
15
14


SCIENCE
EXPERIMENT
STEAM
BUCKLE
CIRCUITS
8+
TRAFFIC LIGHTS
OFF
ON
4.5V


SCIENCE
EXPERIMENT
TO IMAGINE
STEAM
PUZZLE GAMES
TO IMAGINE
TRAFFIC LIGHTS
BUCKLE
CIRCUITS
8+
AGES
OFF
ON
15
14
2
4
As shown in the figure,Turn on the switch 15, the traffic light L1
will start. The time of red and green is 9 seconds respectively,
and the time of yellow is 3 seconds.
Press the press switch 14, will switch to the next light.
-01-